

---

# EFFECTIVE OR RMS VOLTAGE TechTips OF A SINUSOID

---

by

**Guillermo Rico**  
[gurico@nsu.edu](mailto:gurico@nsu.edu)

**Department of Engineering Technology  
New Mexico State University**

In most, if not all, engineering technology electric circuit books, we are told that the effective or root-mean-square (*rms*) voltage of a sinusoid is obtained from the peak voltage through a formula that can be derived “using calculus.” They mention of course that the *rms* value is the equivalent dc voltage that would produce the same average power. This Tech Tip illustrates another technique for obtaining the relationship between *rms* and peak voltage through the use of the power formula and a trigonometric identity.

Let us consider a resistor  $R$  connected across an ac source given by

$$v = V_p \sin \omega t$$

The instantaneous power will then be

$$p = \frac{v^2}{R} = \frac{V_p^2}{R} \sin^2 \omega t$$

Using the trigonometric identity  $\sin^2 x = \frac{1}{2}(1 - \cos 2x)$ , we write

$$p = \frac{V_p^2}{2R}(1 - \cos 2\omega t) = \frac{V_p^2}{2R} - \frac{V_p^2}{2R} \cos 2\omega t$$

Clearly, the average power of this expression is  $V_p^2/2R$  since the average value of the cosine wave is zero; in other words, it is the “dc” portion of the waveform. To better see this, if we make a plot of the power versus time for  $V_p = 1$  V,  $R = 1$   $\Omega$  and  $f = 1$  kHz, as shown in Figure 1, we can see that it is an inverted cosine wave with twice the frequency and oscillating between zero and 1 W. The center of the oscillation is 0.5 W, which is the average value. As expected, the

instantaneous power is always positive and is zero at the zero-crossing points of the sinusoidal voltage.

Equating the power delivered by a dc source to the average power delivered by the ac source using the same resistor  $R$ , we write

$$\frac{V_{dc}^2}{R} = \frac{V_p^2}{2R}$$

Canceling  $R$  and getting the square root of both sides, we obtain the known relationship

$$V_{dc} = \frac{1}{\sqrt{2}}V_p = 0.707V_p = V_{rms}$$

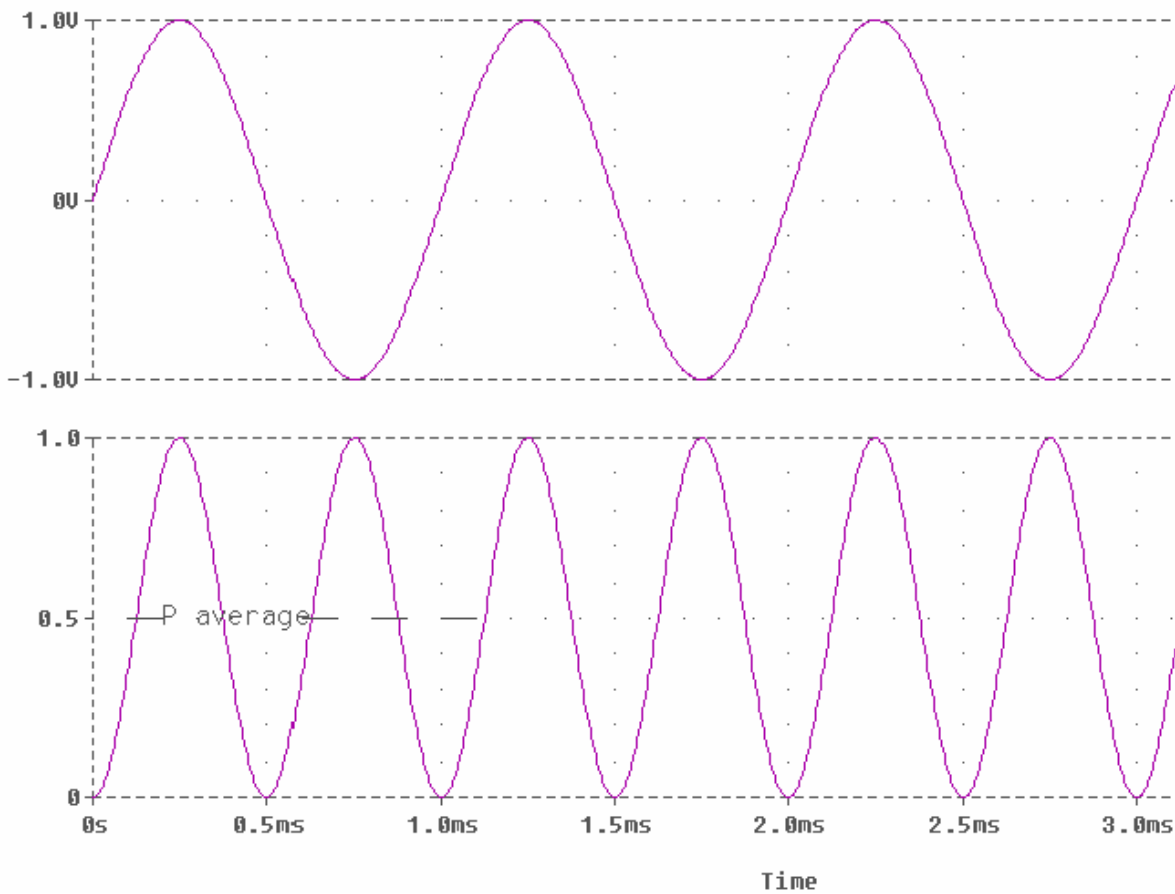


Figure 1. Voltage and power for  $V_p = 1$  V,  $R = 1\Omega$ , and  $f = 1$  kHz